

Contents

Title	Content	Pg. No.
	Declaration by Research Scholar - Originality of Research Work	I
	Certificate of Supervisor	II
	Thesis Approval Form	III
	Declaration by Research Scholar - Submission of Thesis	IV
	Acknowledgement	V
	Contents	VI
	List of Figures	VIII
	List of Tables	X
	Abstract	XI
Chapter : 1	Introduction	1
	1.1 Introduction	1
	1.3 Organization of the Thesis	3
Chapter : 2	Literature Review	4
	2.1 Literature Review	4
	2.2 Research Gap	6
Chapter : 3	Proposed fault-tolerant structure for cascaded H-bridge multilevel inverter	7
	3.1 Mode-0: All modules healthy	10
	3.2 One module faulty; Two modules healthy	11
	3.3 Two modules faulty; One module healthy	18
Chapter : 4	Simulation Results	24
	4.1 Power Circuit	25
	4.2 Fault Detection Logic	29
	4.3 Function block to operate respective relay	31
	4.4 Sub system (SUB-5) to switch respective IGBT	32
	4.5 Simulation Results	33
Chapter : 5	Hardware Development	43
	5.1 Block Diagram	43
	5.2 STM32F407VGT6 Microcontroller	44
	5.3 Relay Card	42

	5.4 Driver Circuit for IGBT	46
	5.5 IGBT Card	49
	5.6 Voltage Sensing Circuit	49
	5.7 Hardware Setup	52
	5.8 Hardware Results for Mode-0	52
	5.9 Hardware Results for Mode-1	54
	5.10 Hardware Results for Mode-2	55
	5.11 Hardware Results for Mode-3	55
	5.12 Hardware Results for Mode-4	56
	5.13 Hardware Results for Mode-5	56
	5.14 Hardware Results for Mode-6	57
Chapter : 6	Hardware Development	58
	6.1 Introduction	58
	6.2 Markov evaluation approach	58
	Conclusion	63
	Bibliography	64
Appendix A	Plagiarism Report	
Appendix B	Publication	

List of Figures

Figure 1.1 Basic cascaded H-bridge multilevel inverter	2
Figure 3.1 Proposed fault-tolerant structure for CHBMLI	8
Figure 3.2 Level-shifted PWM (LS-PWM)	10
Figure 3.3 Current flow under Mode-0	12
Figure 3.4 Current flow during Mode-1	14
Figure 3.5 Current flow during Mode-2	16
Figure 3.6 Current flow during Mode-3	17
Figure 3.7 LS-PWM for Double Module Fault	18
Figure 3.8 Current flow during Mode-4	20
Figure 3.9 Current flow during Mode-5	22
Figure 3.10 Current flow under Mode-6	23
Figure 4.1 MATLAB Simulation	25
Figure 4.2 Power circuit with relays	23
Figure 4.3 Sub system (SUB-1)	26
Figure 4.4 Sub system (SUB-2)	27
Figure 4.5 Sub system (SUB-3)	28
Figure 4.6 Sub system (SUB-4)	29
Figure 4.7 Single module fault detection logic	30
Figure 4.8 Double module fault detection logic	31
Figure 4.9 Function block to operate respective relay	32
Figure 4.10 Sub system (SUB-5) to switch respective IGBT	32
Figure 4.11 Sub system (SUB-5) logic circuit	33
Figure 4.12 Output voltage waveforms under Mode-0	33
Figure 4.13 Output voltage waveforms under Mode-1	35
Figure 4.14 Output voltage waveforms under Mode-2	36
Figure 4.15 Output voltage waveforms under Mode-3	36
Figure 4.16 Output voltage waveforms under Mode-4	37
Figure 4.17 Output voltage waveforms under Mode-5	39

Figure 4.18 Output voltage waveforms under Mode-6	40
Figure 4.19 LS-PWM	41
Figure 4.20 Output Voltage under Mode-5 (Modulation Index 0.7)	42
Figure 5.1 Block Diagram	44
Figure 5.2 STM32F407VGT6 Microcontroller	44
Figure 5.3 Layout of Relay Card	45
Figure 5.4 Relay Card	47
Figure 5.5 Layout of Driver Card for IGBT	48
Figure 5.6 Driver Card for IGBT	49
Figure 5.7 Layout of IGBT Card	50
Figure 5.8 IGBT Card	51
Figure 5.9 Voltage sensing circuit	51
Figure 5.10 Hardware Setup	52
Figure 5.11 Gate Pulses for IGBT of Module-A in Mode-0	52
Figure 5.12 Gate Pulses for IGBT of Module-B in Mode-0	53
Figure 5.13 Gate Pulses for IGBT of Module-C in Mode-0	53
Figure 5.14 Output Voltages under Mode-0	54
Figure 5.15 Output Voltages under Mode-1	54
Figure 5.16 Output Voltages under Mode-2	55
Figure 5.17 Output Voltages under Mode-3	55
Figure 5.18 Output Voltages under Mode-4	56
Figure 5.19 Output Voltages under Mode-5	56
Figure 5.20 Output Voltages under Mode-6	57
Figure 6.1 Markov chain of cascaded H-bridge 7-level inverter	58
Figure 6.2 Markov chain of proposed FT cascaded H-bridge 7-level inverter	59
Figure 6.3 Comparison of reliability f FT-CHBMLI and CHBMLI	62

List of Tables

Table 3.1 Operating modes	7
Table 3.2 Switching of relays under various modes	9
Table 3.3 State selection for IGBT switching	10
Table 3.4 Switching of IGBT Under Mode-0	11
Table 3.5 One module faulty; Two modules healthy	11
Table 3.6 Switching of IGBT Under Mode-1	13
Table 3.7 Switching of IGBT Under Mode-2	15
Table 3.8 Switching of IGBT Under Mode-3	15
Table 3.9 Two modules faulty; One module healthy	18
Table 3.10 Switching of IGBT Under Mode-4	19
Table 3.11 Switching of IGBT Under Mode-5	21
Table 3.12 Switching of IGBT Under Mode-6	21
Table 4.1 List of elements	26
Table 4.2 Connection Possibility of Logical Relay in SUB-1	27
Table 4.3 Connection Possibility of Logical Relay in SUB-2	28
Table 4.4 Connection Possibility of Logical Relay in SUB-3	28
Table 4.5 Fault detection	30
Table 4.6 Switching of IGBT Under Mode-0	34
Table 4.7 Switching of IGBT Under Mode-1	35
Table 4.8 Switching of IGBT Under Mode-2	36
Table 4.9 Switching of IGBT Under Mode-3	37
Table 4.10 Switching of IGBT Under Mode-4	38
Table 4.11 Switching of IGBT Under Mode-5	39
Table 4.12 Switching of IGBT Under Mode-6	40
Table 4.13 State selection for IGBT switching	41
Table 5.1 Pin connection for relays	46
Table 5.2 Pin connection for IGBT	46